

# ECSE 597: Circuit Simulations and Modeling

Assignment 3, October 3, 2019

Wenjie Wei, 260685967

## 1 Chebychev Filter

MATLAB code listings will be presented at the end of the document. Figures 1 and 2 below show the magnitude and angular response of the Chebychev filter.

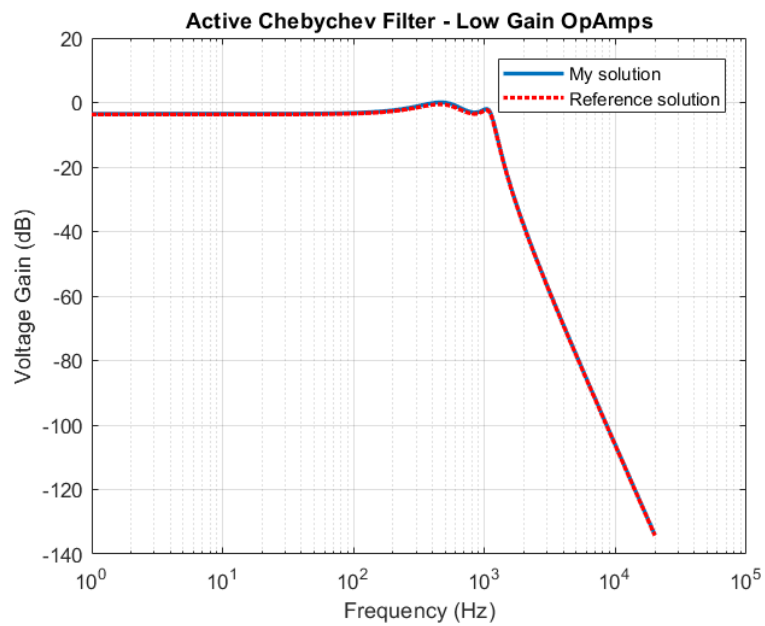


Figure 1: Magnitude Response of the Chebychev Filter

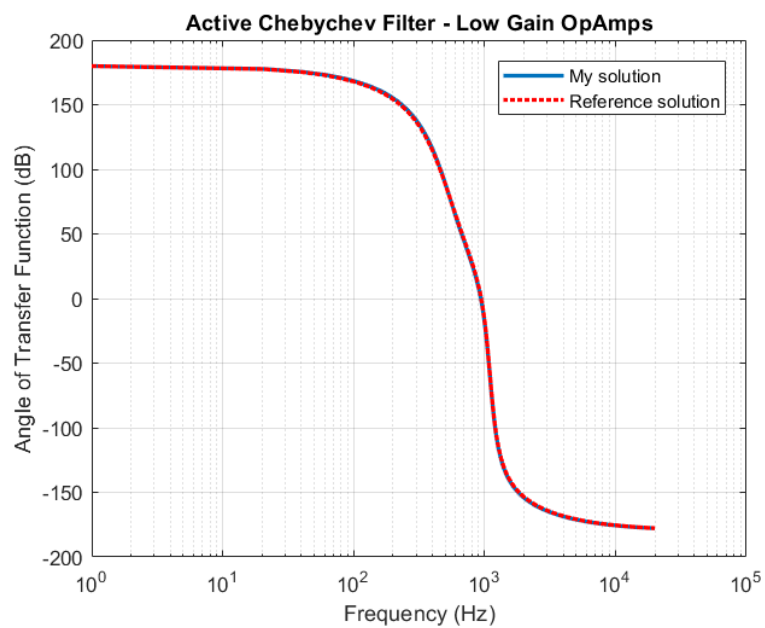


Figure 2: Angular Response of the Chebychev Filter

## 2 Large Gain Chebychev Filter

Figures 3 and 4 below show the magnitude and angular response of the large gain Chebychev filter.

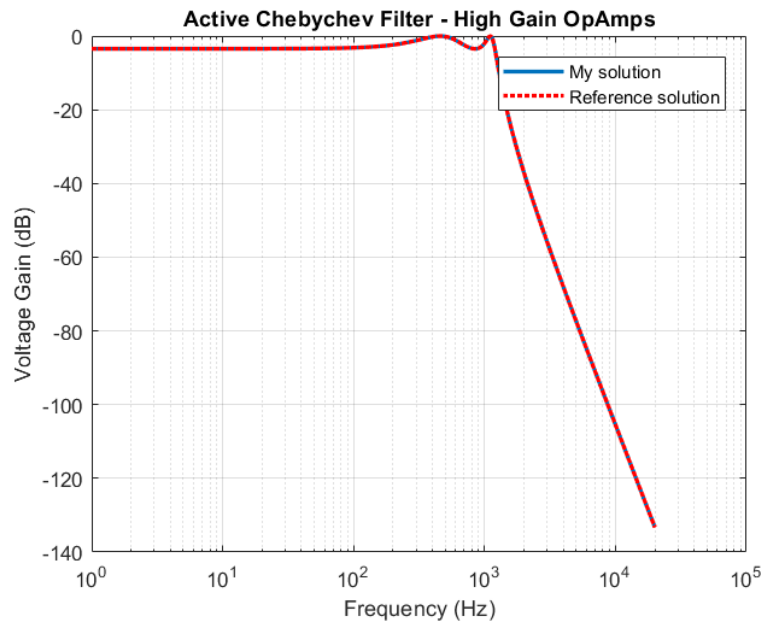


Figure 3: Magnitude Response of the Large Gain Chebychev Filter

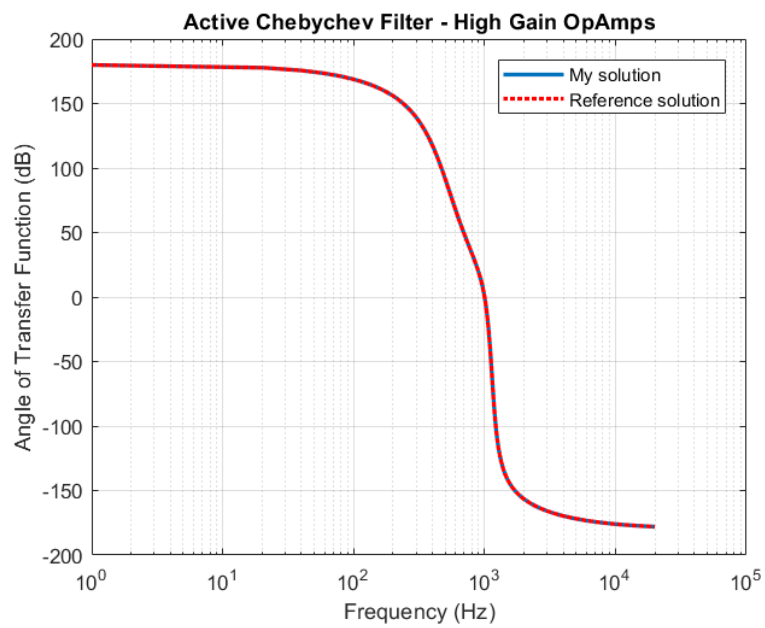


Figure 4: Angular Response of the Large Gain Chebychev Filter

### 3 Circuit 4 Test Bench

Figures 5 and 6 below show the magnitude and angular response of the Circuit 4 Test Bench.

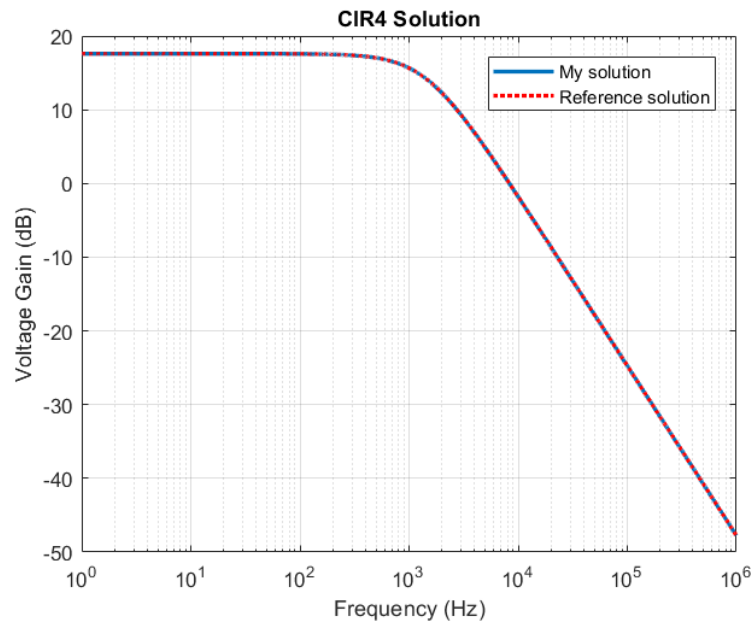


Figure 5: Magnitude Response of the Circuit 4 Test Bench

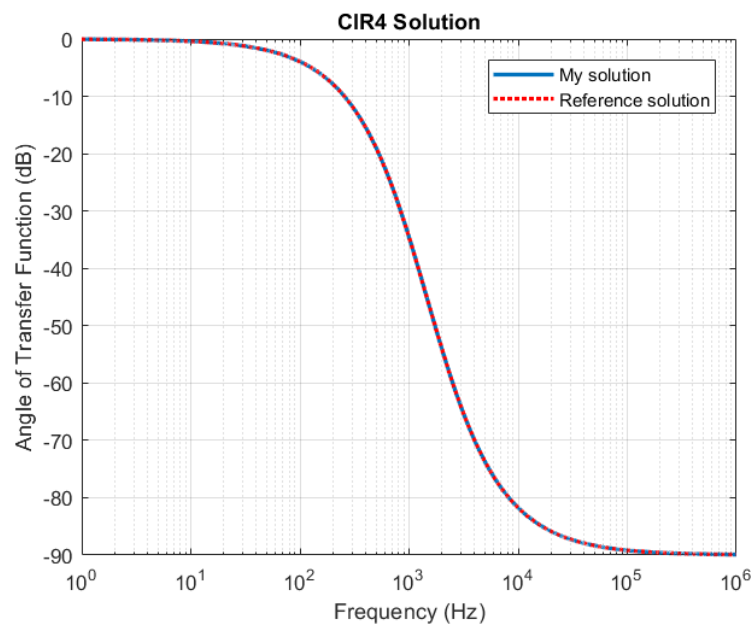


Figure 6: Angular Response of the Circuit 4 Test Bench

## 4 LC Filter 1 Test Bench

Figures 7 and 8 below show the magnitude and angular response of the LC Filter 1 Test Bench.

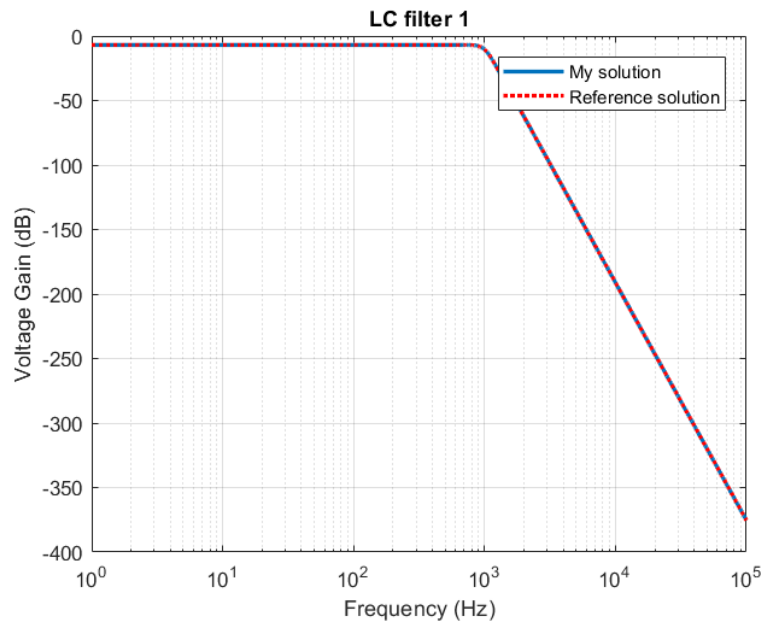


Figure 7: Magnitude Response of the LC Filter 1 Test Bench

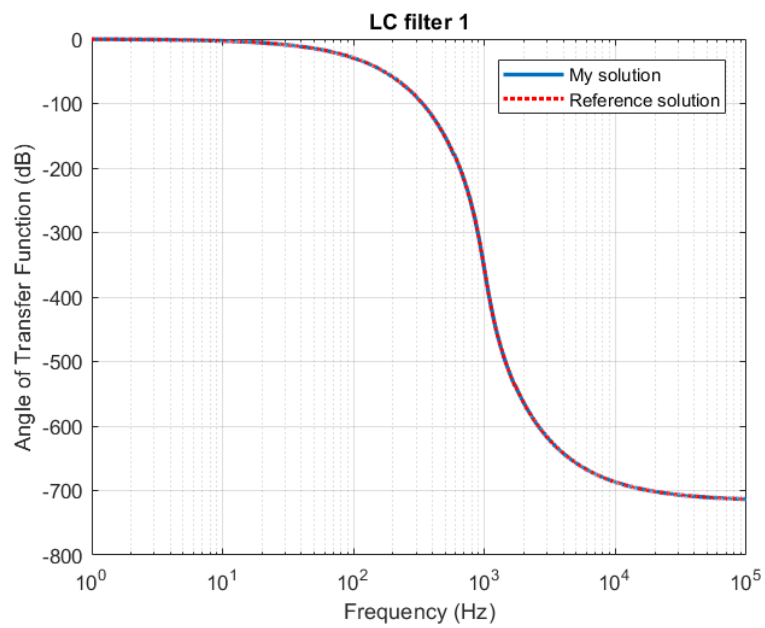


Figure 8: Angular Response of the LC Filter 1 Test Bench

## 5 LC Filter 2 Test Bench

Figures 9 and 10 below show the magnitude and angular response of the LC Filter 2 Test Bench.

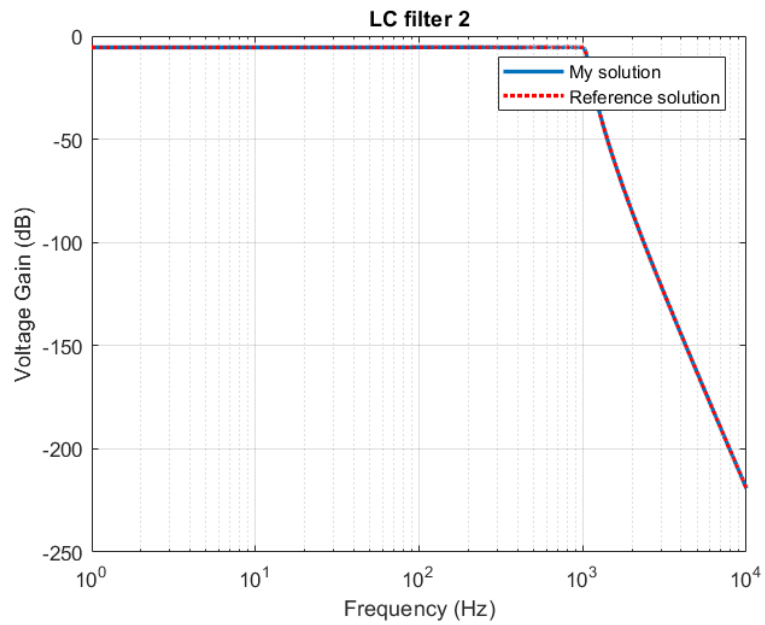


Figure 9: Magnitude Response of the LC Filter 2 Test Bench

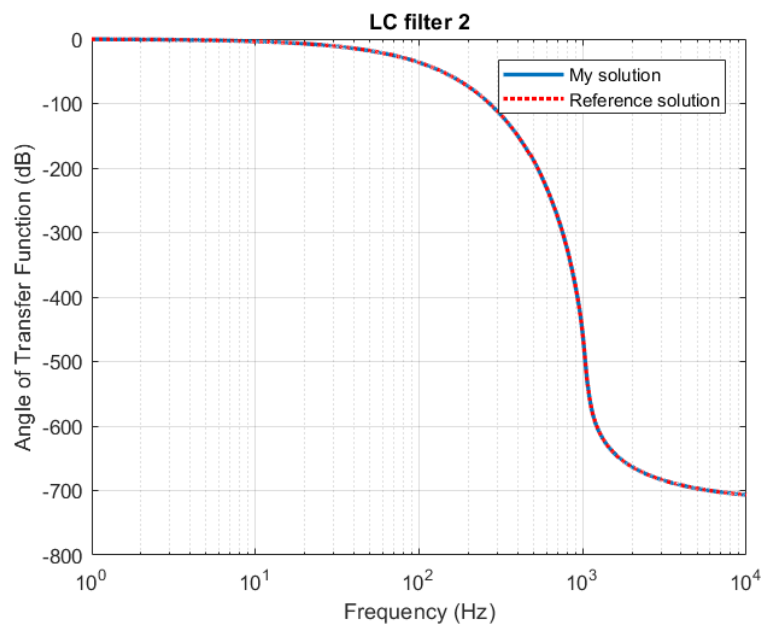


Figure 10: Angular Response of the LC Filter 2 Test Bench

## 6 LC Filter 3 Test Bench

Figures ?? and 12 below show the magnitude and angular response of the LC Filter 3 Test Bench.

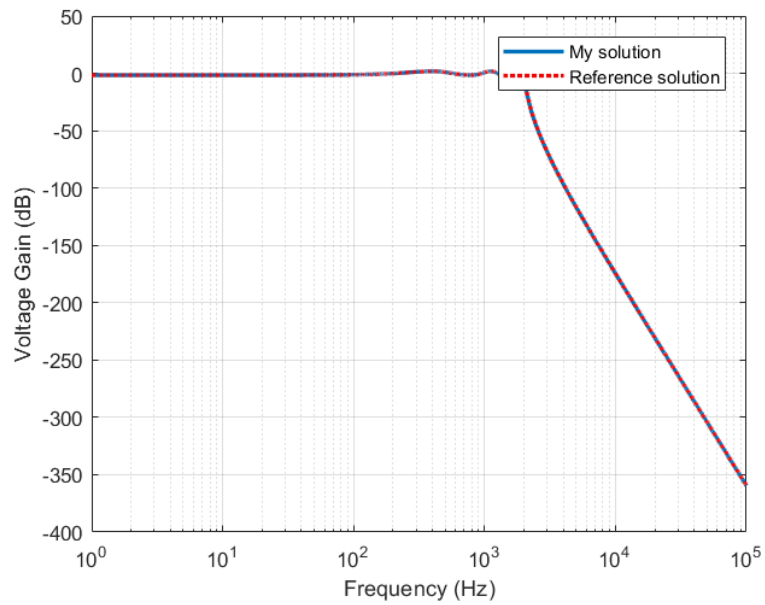


Figure 11: Magnitude Response of the LC Filter 3 Test Bench

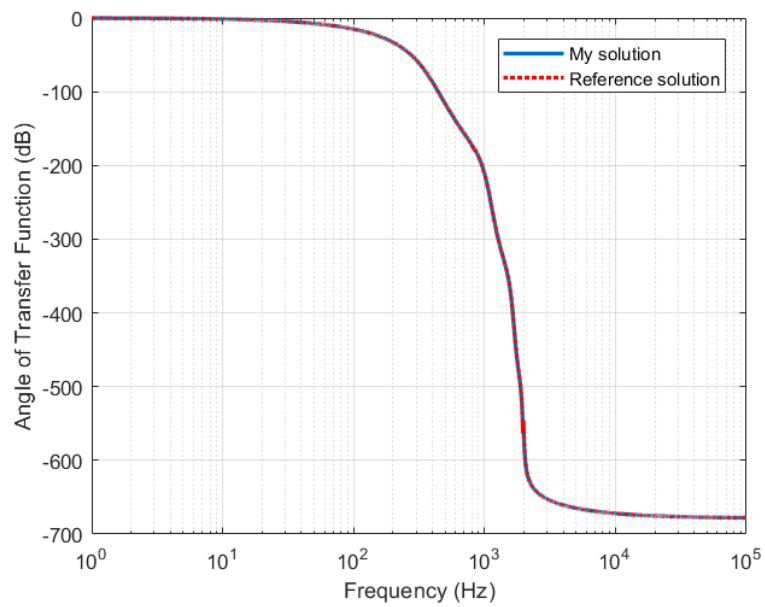


Figure 12: Angular Response of the LC Filter 3 Test Bench

## A Code Listings

*Listing 1: MATLAB Function to Compute the Frequency Response (fsolve.m).*

```

1 function r = fsolve(fpoints ,out)
2 % fsolve(fpoints ,out)
3 % Obtain frequency domain response
4 % global variables G C b
5 % Inputs: fpoints is a vector containing the fequency points at which
6 %         to compute the response in Hz
7 %         out is the output node
8 % Outputs: r is a vector containing the value of
9 %          of the response at the points fpoint
10 %
11     global G C b
12
13     r = zeros(1, size(fpoints, 2));
14
15     for i = 1:size(fpoints, 2)
16         X = (G + 2 * pi * fpoints(i) * 1j * C) \ b;
17         r(1, i) = X(out);
18     end
19 end

```

*Listing 2: MATLAB Function to Generate Inductance Matrices (ind.m).*

```

1 function ind(n1,n2,val)
2     % ind(n1,n2,val)
3     % Add stamp for inductor to the global circuit representation
4     % Inductor connected between n1 and n2
5     % The inductance is val in Henry
6     % global G
7     % global C
8     % global b
9     % Date:
10
11     % defind global variables
12     global G
13     global b
14     global C
15
16     % Add additional entries to G, C, and b matrices.
17     G(end + 1, :) = 0;
18     G(:, end + 1) = 0;
19     C(end + 1, :) = 0;
20     C(:, end + 1) = 0;
21     b(end + 1) = 0;
22
23     % Modify the G matrix.
24     if n1 ~= 0
25         G(end, n1) = 1;
26         G(n1, end) = 1;
27     end
28
29     if n2 ~= 0
30         G(end, n2) = -1;
31         G(n2, end) = -1;
32     end
33
34     % Modify the C matrix.
35     C(end, end) = -val;
36 end
37

```

*Listing 3: MATLAB Function to Generate VCCS Matrices (vccs.m).*

```

1  function vccs(nd1,nd2,ni1,ni2,val)
2      % vccs(nd1,nd2,ni1,ni2,val)
3      % Add stamp for voltage controlled current source
4      % to the global circuit representation
5      % ni1 and ni2 are the controlling voltage nodes
6      % the controlled current source is between nd1 and nd2
7      % The controlled current (from nd1 to nd2) is val*(Vni1-Vni2)
8
9
10     global G
11
12     if nd1 ~= 0
13         if ni1 ~= 0
14             G(nd1, ni1) = G(nd1, ni1) + val;
15         end
16         if ni2 ~= 0
17             G(nd1, ni2) = G(nd1, ni2) - val;
18         end
19     end
20
21     if nd2 ~= 0
22         if ni1 ~= 0
23             G(nd2, ni1) = G(nd2, ni1) - val;
24         end
25         if ni2 ~= 0
26             G(nd2, ni2) = G(nd2, ni2) + val;
27         end
28     end
29 end

```

*Listing 4: MATLAB Function to Generate VCVS Matrices (vccs.m).*

```

1  function vcvs(nd1,nd2,ni1,ni2,val)
2      % vcvs(nd1,nd2,ni1,ni2,val)
3      % Add stamp for a voltage controlled voltage source
4      % to the global circuit representation
5      % val is the gain of the vcvs
6      % ni1 and ni2 are the controlling voltage nodes
7      % nd1 and nd2 are the controlled voltage nodes
8      % The relation of the nodal voltages at nd1, nd2, ni1, ni2 is:
9      %  $V_{nd1} - V_{nd2} = val \cdot (V_{ni1} - V_{ni2})$ 
10
11
12     global G
13     global b
14     global C
15
16     % Extend the matrices.
17     G(end + 1, :) = 0;
18     G(:, end + 1) = 0;
19     b(end + 1) = 0;
20     C(end + 1, :) = 0;
21     C(:, end + 1) = 0;
22
23     if nd1 ~= 0
24         G(nd1, end) = 1;
25         G(end, nd1) = 1;
26     end
27
28     if nd2 ~= 0
29         G(nd2, end) = -1;
30         G(end, nd2) = -1;
31     end
32
33     if ni1 ~= 0
34         G(end, ni1) = -val;
35     end
36     if ni2 ~= 0
37         G(end, ni2) = val;

```



```
38     end
39 end
40
41
42
43
44
45
```